

Practical 4

Name: Pratiksha Madhav Basawade

Roll no: E43017

Division: BE-III

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_arith.ALL;
```

```
use IEEE.STD_LOGIC_unsigned.ALL;
```

```
entity fifo is
```

```
    Port ( enr,enwr,clk,reset : in  STD_LOGIC;
```

```
          datain : in  STD_LOGIC_VECTOR (3 downto 0);
```

```
          dataout : out  STD_LOGIC_VECTOR (3 downto 0);
```

```
          full,empty : out  STD_LOGIC);
```

```
end fifo;
```

```
architecture Behavioral of fifo is
```

```
type memory_type is array (0 to 7)of STD_LOGIC_VECTOR (3 downto 0);
```

```
signal memory: memory_type;
```

```
signal readptr,writeptr:STD_LOGIC_VECTOR (3 downto 0):="0000";
```



```
begin
```

```
process(clk,reset)
```

```

begin
if (reset='1') then dataout<="0000";
else
if (clk'event and clk='1' and enr<='0' and enwr<='1') then
memory(conv_integer(writeptr))<=datain;
writeptr<=writeptr+'1';
end if;
if (clk'event and clk='1' and enr<='1' and enwr<='0') then
dataout<=memory(conv_integer(readptr));
readptr<=readptr+'1';
end if;
if readptr="0000" then
empty<='1';
else empty<='0';
end if;
if writeptr="0111" then
full<='1';
else full<='0';
end if;
end if;
end process;
end Behavioral;

```

  

testbench

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY sss IS
```

```
END sss;
```

```
ARCHITECTURE behavior OF sss IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT fifo
```

```
PORT(
```

```
    enr : IN  std_logic;
```

```
    enwr : IN  std_logic;
```

```
    clk : IN  std_logic;
```

```
    reset : IN  std_logic;
```

```
    datain : IN  std_logic_vector(3 downto 0);
```

```
    dataout : OUT  std_logic_vector(3 downto 0);
```

```
    full : OUT  std_logic;
```

```
    empty : OUT  std_logic
```

```
);
```

```
END COMPONENT
```

```
--Inputs
```

```
signal enr : std_logic := '0';  
signal enwr : std_logic := '0';  
signal clk : std_logic := '0';  
signal reset : std_logic := '0';  
signal datain : std_logic_vector(3 downto 0) := (others => '0');
```

--Outputs

```
signal dataout : std_logic_vector(3 downto 0);  
signal full : std_logic;  
signal empty : std_logic;
```

-- Clock period definitions

```
constant clk_period : time := 10 ns;
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: fifo PORT MAP (  
    enr => enr,  
    enwr => enwr,  
    clk => clk,  
    reset => reset,  
    datain => datain,  
    dataout => dataout,  
    full => full,
```

```

        empty => empty
    );

-- Clock process definitions
clk_process :process
begin

    clk <= '0';

    wait for clk_period/2;

    clk <= '1';

    wait for clk_period/2;

end process;

-- Stimulus process
stim_proc: process
begin

enwr<='1'; enr<='0';

datain<="0001"    ;

    -- hold reset state for 100 ns.

    wait for 10 ns;

datain<="0010";

    -- hold reset state for 100 ns.

    wait for 10 ns;

datain<="0100"    ;

    -- hold reset state for 100 ns.

    wait for 10 ns;

```

```

        datain<="1000";

-- hold reset state for 100 ns.

wait for 10 ns;

        datain<="0011"    ;

-- hold reset state for 100 ns.

wait for 10 ns;

datain<="0111";

-- hold reset state for 100 ns.

wait for 10 ns;

        datain<="1111";

-- hold reset state for 100 ns.

wait for 10 ns;

        datain<="1001";

-- hold reset state for 100 ns.

wait for 10 ns;

enwr<='0'; enr<='1';

wait for 80 ns;

wait for clk_period*10;


-- insert stimulus here

wait;

end process;

END

```

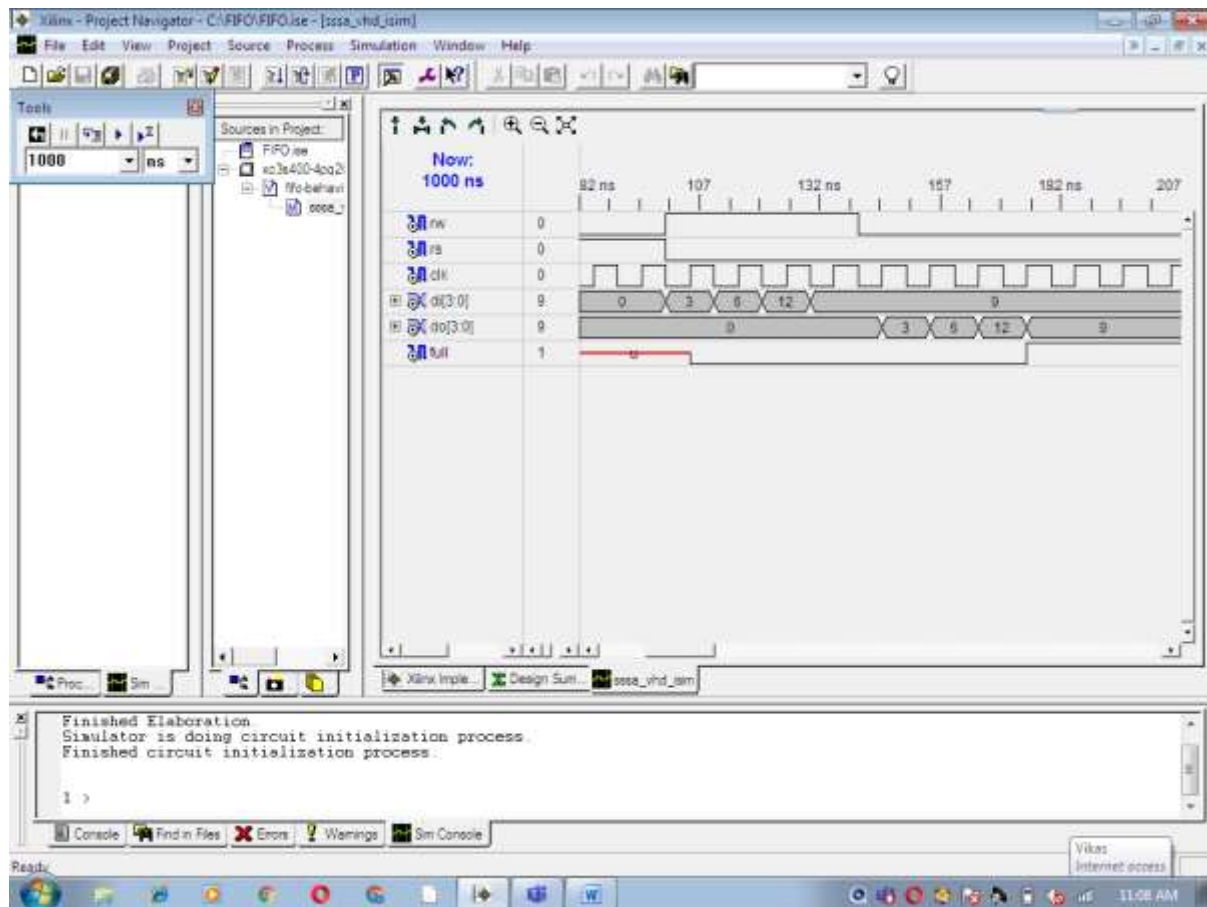

CLOCK DIVISION

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_arith.ALL;

use IEEE.STD_LOGIC_unsigned.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity fifo is

Port (enr,enwr,clk,reset : in STD_LOGIC;

datain : in STD_LOGIC_VECTOR (3 downto 0);

dataout : out STD_LOGIC_VECTOR (3 downto 0);

full,empty : out STD_LOGIC);

end fifo;

architecture Behavioral of fifo is

type memory_type is array (0 to 7)of STD_LOGIC_VECTOR (3 downto 0);

signal memory: memory_type;

signal clk1: std_logic;

signal count : std_logic_vector(20 downto 0);

signal readptr,writeptr:STD_LOGIC_VECTOR (3 downto 0):="0000";

begin

process(clk)

begin

if(clk'event and clk='1') then

count<=count+1;

end if;

```

clk1<=count(20);
end process;
process(clk1)
begin
--if (reset='1') then dataout<="0000";
--else

if (clk1'event and clk1='1' and enr<='0' and enwr<='1') then
memory(conv_integer(writeptr))<=datain;
writeptr<=writeptr+'1';
end if;

if (clk1'event and clk1='1' and enr<='1' and enwr<='0') then
dataout<=memory(conv_integer(readptr));
readptr<=readptr+'1';
end if;

if readptr="0000" then
empty<='1';
else empty<='0';
end if;

if writeptr="0111" then
full<='1';

```

```
else full<='0';  
end if;  
--end if;  
end process;
```

```
end Behavioral;
```

```
UCF FILE
```

```
net clk loc=p183;  
net reset loc=p102;  
net enr loc=p101;  
net enwr loc=p87;  
net datain(0) loc=p80;  
net datain(1) loc=p78;  
net datain(2) loc=p77;  
net datain(3) loc=p74;  
net dataout(0) loc=p168;  
net dataout(1) loc=p171;  
net dataout(2) loc=p172;  
net dataout(3) loc=p175;  
net full loc=p154;  
net empty loc=p161;
```