

## Practical No -: 10

### HALF ADDER -:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity HALFADDER is

    Port ( A : in STD_LOGIC;

           B : in STD_LOGIC;

           SUM : out STD_LOGIC;

           CARRY : out STD_LOGIC);

end HALFADDER;


architecture Behavioral of HALFADDER is


begin

    SUM<=A XOR B;

    CARRY<= A AND B;

end Behavioral;
```

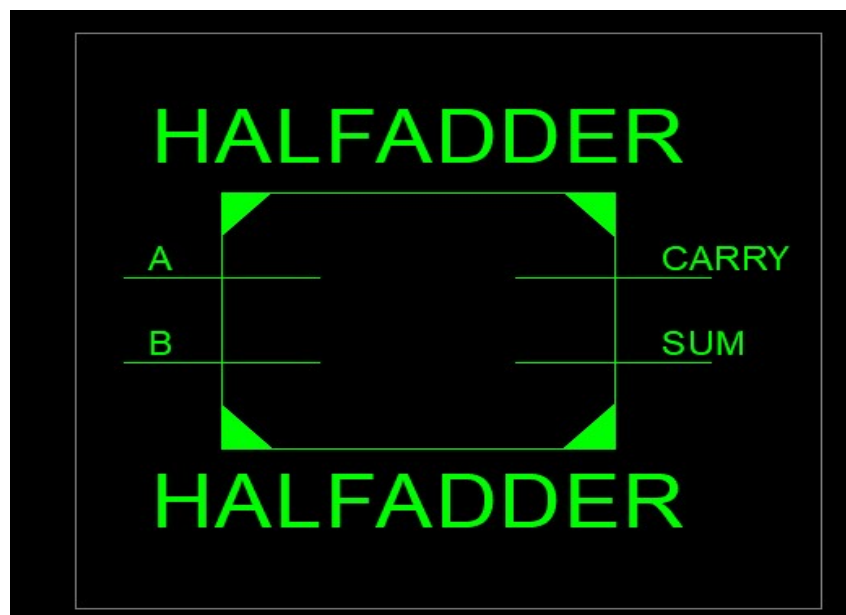

 

### FULL ADDER -:

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity FULLADDER is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

CIN : in STD\_LOGIC;

SUM : out STD\_LOGIC;

COUT : out STD\_LOGIC);

end FULLADDER;

architecture Behavioral of FULLADDER is

begin

component HALFADDER

port( A : in   STD\_LOGIC;

        B : in   STD\_LOGIC;

        SUM : out   STD\_LOGIC;

        CARRY : out   STD\_LOGIC);

end component;

signal S1,C1,C2:STD\_LOGIC;


begin


ha1:HALFADDER port map (A,B,S1,C1);

ha2:HALFADDER port map (S1,CIN,SUM,C2);

COUT<=C1 OR C2;

end Behavioral;

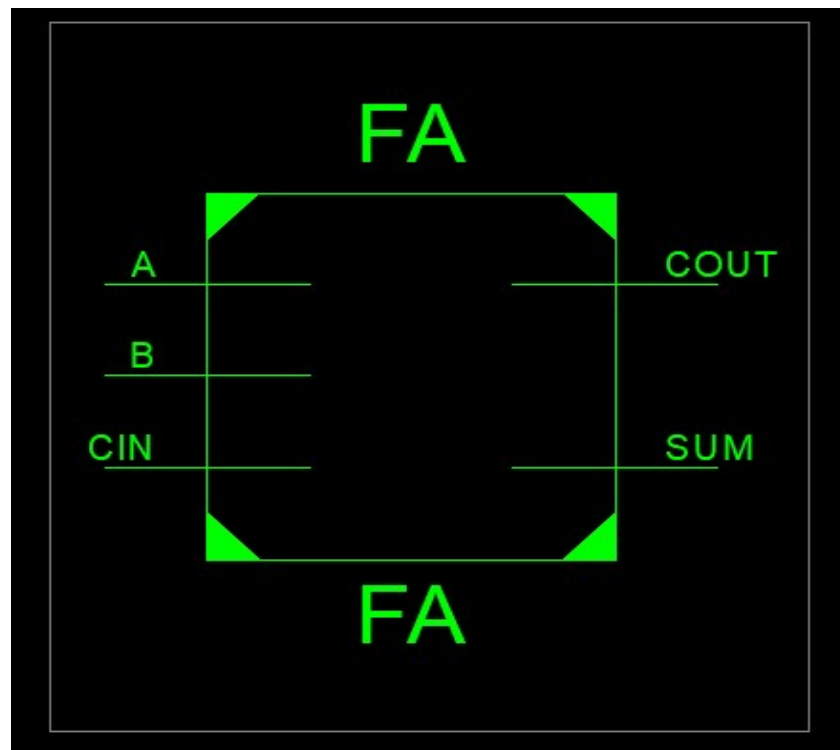

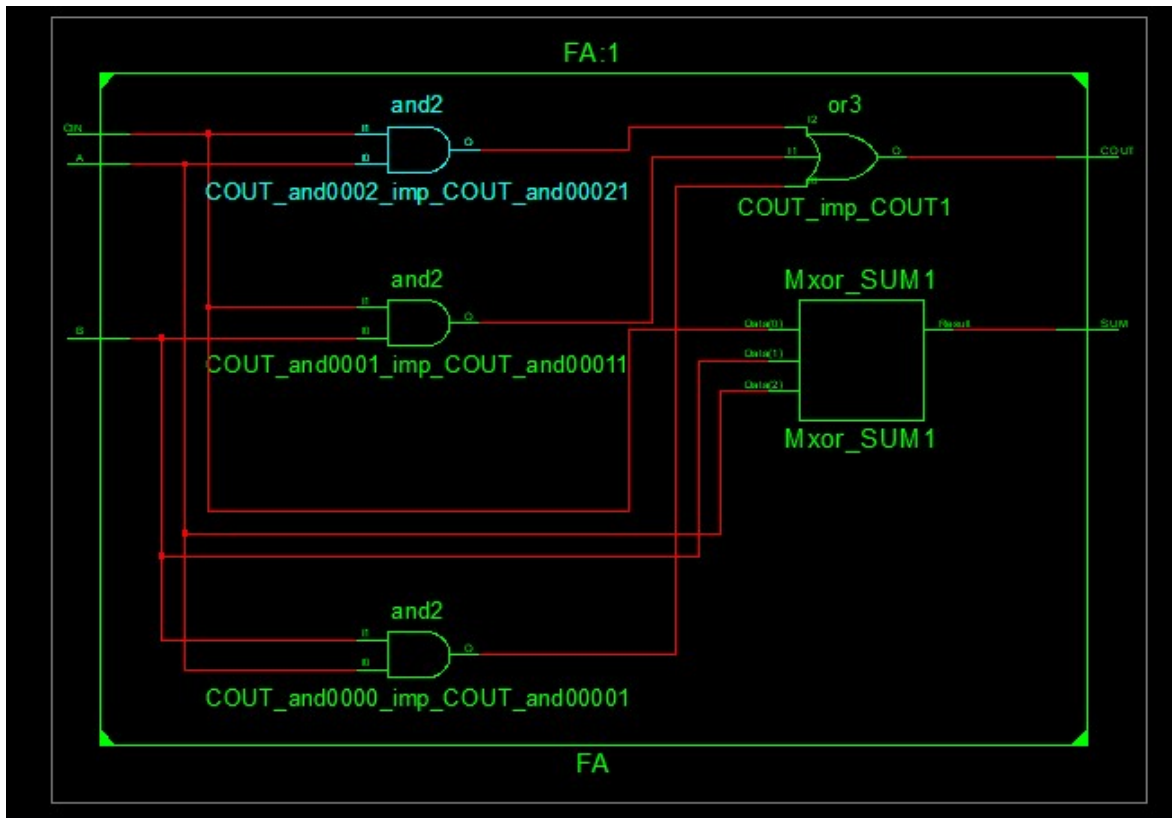

## TESTBENCH -:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY FAA IS
```

```
END FAA;
```

```
ARCHITECTURE behavior OF FAA IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT FA
```

```
PORT(
```

```
    A : IN    std_logic;
```

```
    B : IN    std_logic;
```

```
    CIN : IN   std_logic;
```

```

        SUM : OUT    std_logic;
        COUT : OUT    std_logic
    );
END COMPONENT;

--Inputs
signal A : std_logic := '0';
signal B : std_logic := '0';
signal CIN : std_logic := '0';

--Outputs
signal SUM : std_logic;
signal COUT : std_logic;
BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: FA PORT MAP (
        A => A,
        B => B,
        CIN => CIN,
        SUM => SUM,
        COUT => COUT );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        A<='0'; B<='0'; CIN<='0';
        wait for 100 ns;
        A<='0'; B<='0'; CIN<='1';

```

```

wait for 100 ns;
A<='0'; B<='1'; CIN<='0';
wait for 100 ns;
A<='0'; B<='1'; CIN<='1';
wait for 100 ns;
A<='1'; B<='0'; CIN<='0';
wait for 100 ns;
A<='1'; B<='0'; CIN<='1';
wait for 100 ns;
A<='1'; B<='1'; CIN<='0';
wait for 100 ns;
A<='1'; B<='1'; CIN<='1';
wait for 100 ns;
wait;
end process;

```

